



For 0-5 Volt CV, replace R1, R2 etc. with wire, and omit R1, R2 etc. and omit R17, R18 etc.

If less voices are needed, opamp buffers can be omitted.

